

Project - Build a Power Bank

1. Design:

1. Use a rechargeable lithium-ion battery, boost converter, and USB output.
2. Add a charging circuit using an IC like TP4056.

2. Assembly and Testing:

1. Solder components to a PCB and test voltage output.